

Circuit Diagram Problems

Answer each question in the space provided. Show all work and box your answer(s).


1. Three resistors are set up in series and connected to a 12-Volt power supply, as in the diagram.

$R_1 = 10\Omega, R_2 = 5\Omega, \text{ and } R_3 = 15\Omega$

- a. What is the total equivalent resistance of this circuit?

$$R_s = R_1 + R_2 + R_3$$

$$= 10 + 5 + 15 = \boxed{30\Omega}$$

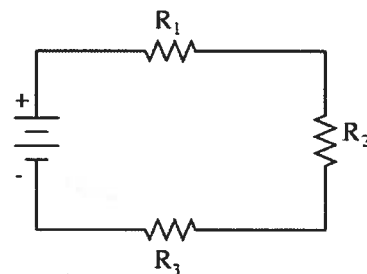

- b. The current running through R_1 is 0.4 Amps. What is the total current of the circuit?

$\boxed{0.4 \text{ Amps}}$ Current is always the same for all components in series.

- c. What is the voltage drop across R_1 ?

$$I_1 = 0.4 \text{ A} \quad V_1 = I_1 R_1$$

$$R_1 = 10\Omega \quad V_1 = (0.4)(10) \rightarrow \boxed{V_1 = 4 \text{ Volts}}$$

2. Three resistors are connected in parallel with a 30-Volt power supply, as in the diagram.


$R_1 = 30\Omega, R_2 = 60\Omega, \text{ and } R_3 = 60\Omega$

- a. What is the equivalent resistance of the whole circuit?

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{30} + \frac{1}{60} + \frac{1}{60} \rightarrow \frac{1}{R_p} = \frac{1}{15}$$

$$\boxed{R_p = 15\Omega}$$

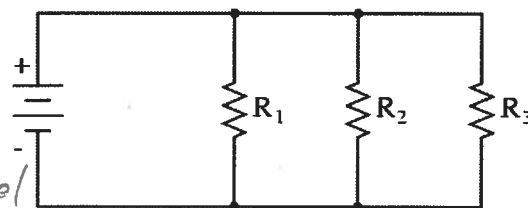

- b. What is the voltage across $R_1, R_2,$ and R_3 ?



$\boxed{30 \text{ V}}$ Voltage is always the same for components in parallel.

- c. What is the current through R_2 ?

$$V_2 = I_2 R_2 \rightarrow I_2 = \frac{V_2}{R_2} = \frac{30}{60} = \boxed{0.5 \text{ A}}$$

$$I_2 = \frac{V_2}{R_2}$$

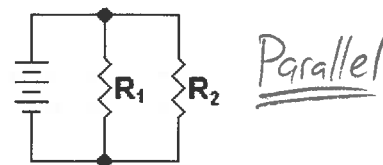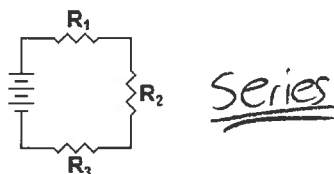3. Fill in the table of values for each circuit.




a)	V	I	R
Total	24.0 V	2 A	12 Ω
R_1	4 V	2 A	2.0 Ω
R_2	12 V	2 A	6.0 Ω
R_3	8 V	2 A	4.0 Ω

↑ all the same


b)	V	I	R
Total	12.0 V	9 A	1.33 Ω
R_1	12 V	6 A	2.0 Ω
R_2	12 V	3 A	4.0 Ω

↑ all the same


Series and Parallel Circuit Problems

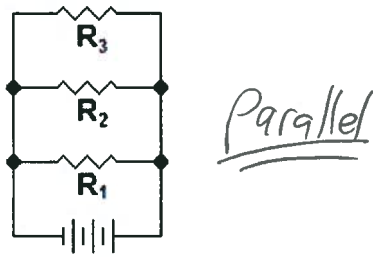


c)	V	I	R
Total	36V	6A	6Ω
R ₁	36V	2.0 A	18Ω
R ₂	36V	3.0 A	12.0 Ω
R ₃	36V	1.0 A	36 Ω

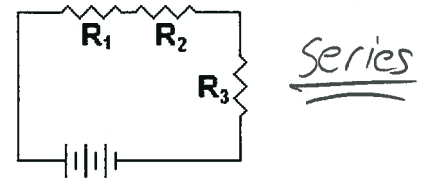

d)	V	I	R
Total	36V	2A	18Ω
R ₁	8V	2.0 A	4.0 Ω
R ₂	12V	2A	6.0 Ω
R ₃	16V	2A	8.0 Ω

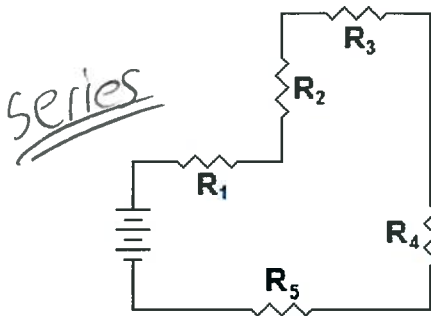

e)	V	I	R
Total	60.0 V	2 A	30Ω
R ₁	16 V	2 A	8.0 Ω
R ₂	24 V	2 A	12.0 Ω
R ₃	8 V	2 A	4.0 Ω
R ₄	8 V	2.0 A	4 Ω
R ₅	4.0 V	2 A	2Ω

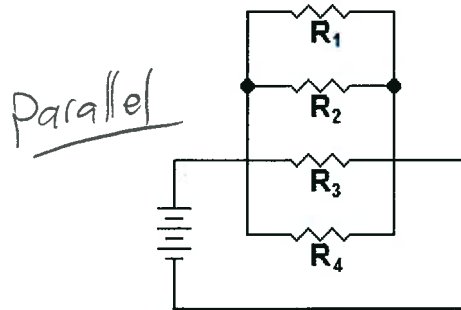

f)	V	I	R
Total	24.0 V	11.27A	2.13Ω
R ₁	24V	8A	3.0 Ω
R ₂	24V	2.67A	9.0 Ω
R ₃	24V	0.3 A	80 Ω
R ₄	24V	0.3 A	80Ω

$$V_s = V_1 + V_2 + V_3 \dots + V_n$$

$$I_s = I_1 = I_2 = I_3 \dots = I_n$$

$$R_s = R_1 + R_2 + R_3 \dots + R_n$$

$$V_p = V_1 = V_2 = V_3 \dots = V_n$$

$$I_p = I_1 + I_2 + I_3 \dots + I_n$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots + \frac{1}{R_n}$$