

Name: KEY

Period: \_\_\_\_\_  
Pre-AP Physics

### Circuit Diagram Problems – Part 2

Answer each question in the space provided. Show all work and box your answer(s).

1. A light bulb with a resistance of 36 Ohms has 0.25 Amperes of current flowing through it.

- a. What is the potential difference (voltage) across the bulb?

$$V = IR$$

$$V = (0.25)(36) \rightarrow \boxed{V = 9 \text{ Volts}}$$

- b. What is its power output?

$$P = IV$$

$$P = (0.25)(9) \rightarrow \boxed{P = 2.25 \text{ Watts}}$$

- c. How much charge flows through the light bulb in one minute?

$$I = \frac{Q}{t} \rightarrow Q = (0.25)(60) \rightarrow 60 \text{ seconds}$$

$$Q = It \rightarrow \boxed{Q = 15 \text{ Coulombs}}$$

2. Roger purchases a blender with a power rating of 20 Watts. He goes home and plugs it into the power outlet in his kitchen, which is 110 Volts.

- a. How much electric current does the blender require in order to operate?

$$P = IV \rightarrow I = \frac{20}{110}$$

$$I = \frac{P}{V} \rightarrow \boxed{I = 0.18 \text{ Amps}}$$


- b. What is its electrical resistance?

$$V = IR \rightarrow R = \frac{110}{0.18}$$


$$R = \frac{V}{I} \rightarrow \boxed{R = 605 \Omega}$$

3. Draw a sketch for each of the following circuits, as they are described:

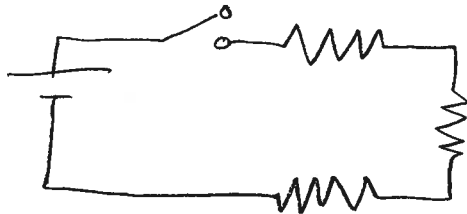
- a. A power source is connected in series with 3 resistors and a switch.



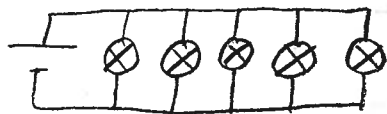- b. Five light bulbs are all connected in parallel with a battery.




- c. A 30.0  $\Omega$  resistor is connected in parallel to a 15.0  $\Omega$  resistor. These are joined in series to a 5.00  $\Omega$  resistor, a switch, and a potential difference of 30.0 V.

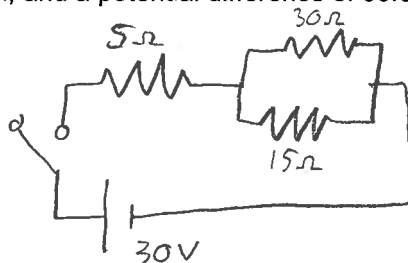


Problems 4-10: Complete the table of values for each circuit.

4.

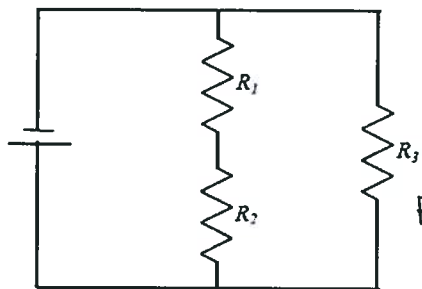


	V	I	R
Battery	12.00 V	2.00 A	6 Ω
R <sub>1</sub>	7.2 V	1.2 A	6.00 Ω
R <sub>2</sub>	4.8 V	1.2 A	4.00 Ω
R <sub>3</sub>	12 V	0.8 A	15.00 Ω

5.

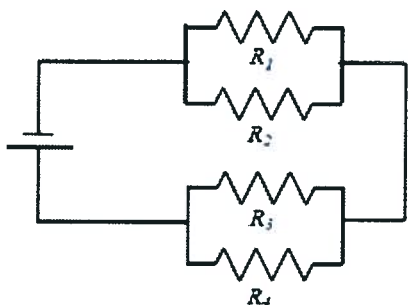


	V	I	R
Battery	36 V	9 A	4 Ω
R <sub>1</sub>	12.00 V	6 A	2.00 Ω
R <sub>2</sub>	12 V	3 A	4.00 Ω
R <sub>3</sub>	24.00 V	6 A	4.00 Ω
R <sub>4</sub>	24 V	3 A	8.00 Ω

6.

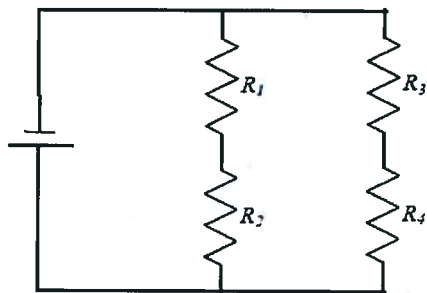


	V	I	R
Battery	50.00 V	5.00 A	10 Ω
R <sub>1</sub>	25 V	2.00 A	12.5 Ω
R <sub>2</sub>	25.00 V	2 A	12.5 Ω
R <sub>3</sub>	10.00 V	3 A	3.33 Ω
R <sub>4</sub>	40 V	3.00 A	13.33 Ω

7.

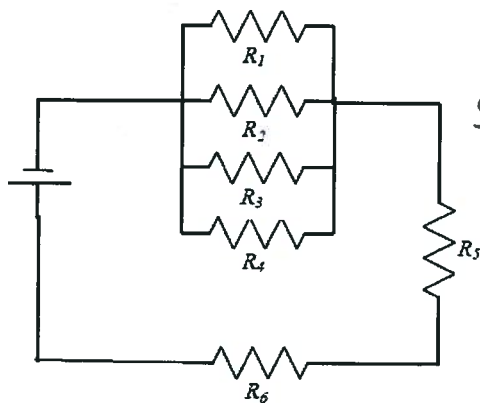


	V	I	R
Battery	65 V	5 A	13 Ω
R <sub>1</sub>	10 V	0.5 A	20.00 Ω
R <sub>2</sub>	10.00 V	1 A	10 Ω
R <sub>3</sub>	10 V	2.5 A	4.00 Ω
R <sub>4</sub>	10 V	1.00 A	10 Ω
R <sub>5</sub>	25 V	5.00 A	5.00 Ω
R <sub>6</sub>	30 V	5 A	6.00 Ω

8.

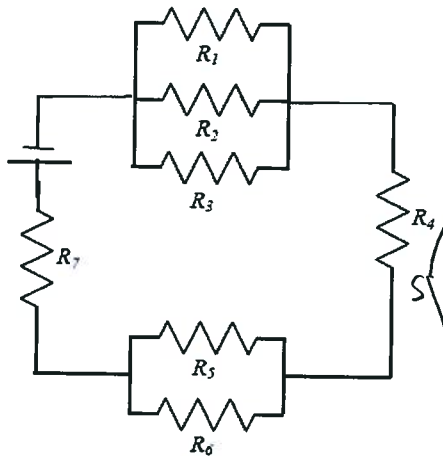


	V	I	R
Battery	80 V	12.00 A	6.67 Ω
R <sub>1</sub>	18 V	4 A	4.5 Ω
R <sub>2</sub>	18.00 V	2.00 A	9 Ω
R <sub>3</sub>	18 V	6 A	3.00 Ω
R <sub>4</sub>	48 V	12 A	4.00 Ω
R <sub>5</sub>	8 V	4 A	2.00 Ω
R <sub>6</sub>	8 V	8.00 A	1 Ω
R <sub>7</sub>	6.00 V	12 A	0.5 Ω

9.

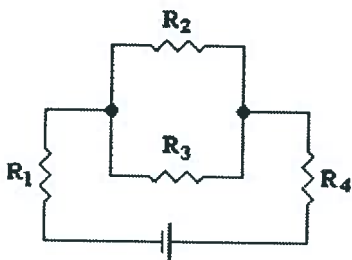

	V	I	R	P
Total	800V	4A	200Ω	3,200 W
R <sub>1</sub>	440V	4A	110Ω	1,760 W
R <sub>2</sub>	96V	2.4A	40Ω	230.4W
R <sub>3</sub>	96V	1.6A	60Ω	153.6 W
R <sub>4</sub>	264V	4A	66Ω	1,056W

10.

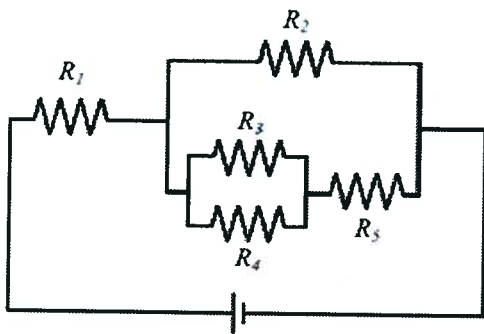

	V	I	R
Battery	24.0 V	2.4A	10 Ω
R <sub>1</sub>	6V	2.4A	2.5 Ω
R <sub>2</sub>	18V	0.9 A	20.0 Ω
R <sub>3</sub>	9V	0.9A	10.0 Ω
R <sub>4</sub>	9.0 V	0.6A	15 Ω
R <sub>5</sub>	9V	1.5 A	6 Ω

$$I = \frac{Q}{t}$$

$$V = IR$$

$$P = IV$$

$$V_S = V_1 + V_2 + V_3 \dots + V_n$$

$$V_P = V_1 = V_2 = V_3 \dots = V_n$$

$$I_S = I_1 = I_2 = I_3 \dots = I_n$$

$$I_P = I_1 + I_2 + I_3 \dots + I_n$$

$$R_S = R_1 + R_2 + R_3 \dots + R_n$$

$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots + \frac{1}{R_n}$$